

TYPES OF DIODE BREAKDOWN

Avalanche breakdown

Under reverse bias,

Voltage increases \longrightarrow Depletion region widens \longrightarrow Accumulation of more immobile ions

Collision with other atomic structures


Kinetic energy is provided to charge carriers

Electric field is generated



Releases more charge carriers;
covalent bonds broken,
electron-hole generating

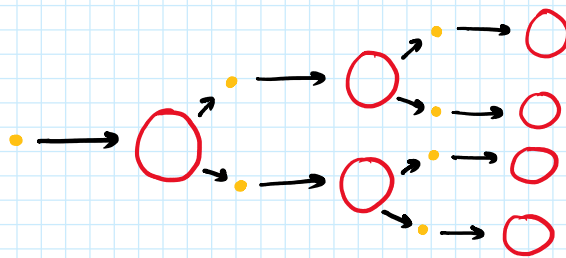- Happens due to impact ionisation / avalanche multiplication?




- Motion of these charge carriers creates a sudden jump in current, often damaging the diode itself

Zener Breakdown

- Occurs in Zener diode \longrightarrow Both p and n heavily doped
- Due to more charge carriers, depletion region becomes narrow
- Smaller reverse bias voltage \longrightarrow stronger electric field



more charge carriers liberated

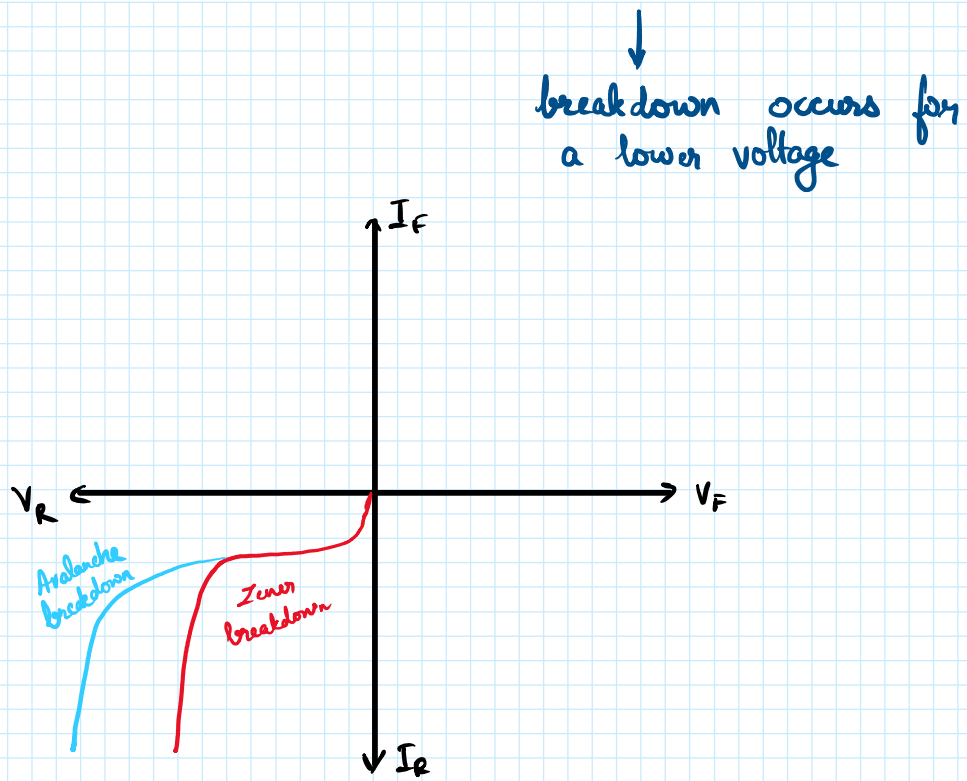

DIODE APPROXIMATIONS / EQUIVALENT DIAGRAMS

Mathematical method to approximate non-linear behaviour of real diodes

three
types

→ First Approximation (Ideal Diode Characteristics)



→ Second Approximation (Simplified Diode Characteristics)

→ Third Approximation (Linear Piece-wise Diode Characteristics)

First Approximation (Ideal Diode Characteristics)


FORWARD BIAS: Closed switch, no voltage drop

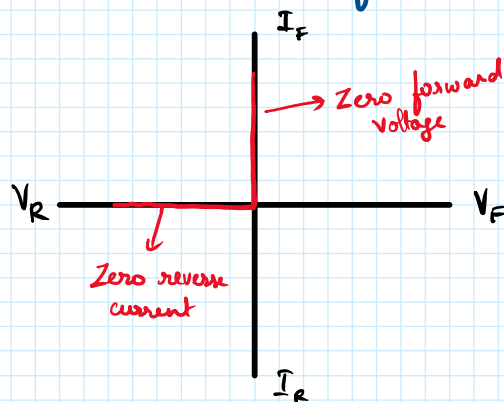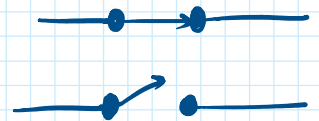REVERSE BIAS: Open switch, infinite resistance




Second Approximation (Simplified Diode Characteristics)

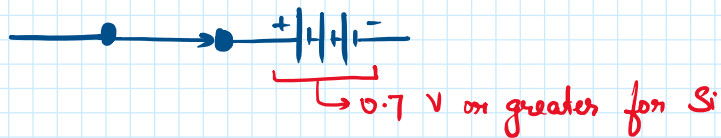FORWARD BIAS: In series with a battery to turn on, specific knee voltage is given




REVERSE BIAS: Open switch

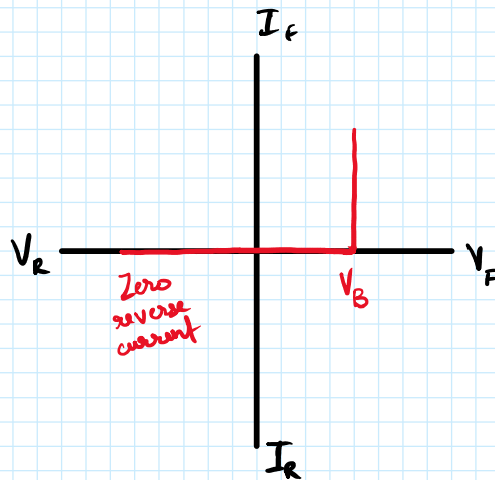

Third Approximation (Linear Piece-wise Diode Characteristics)

FORWARD: Includes knee voltage as well as voltage across bulk resistance R_B
Voltage drop V_D

$$V_D = 0.7V + (I_D)(R_B)$$

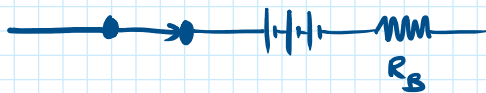

REVERSE: Open switch with R_B in parallel

