

## 6. Logical Operations, Transistors


21 September 2023 09:42

### LOGICAL OPERATIONS

#### • OR GATE

A	B	Y
0	0	0
1	0	1
0	1	1
1	1	1

Binary levels from voltage	
1	→ 4-5V (say)
0	→ 0-1V

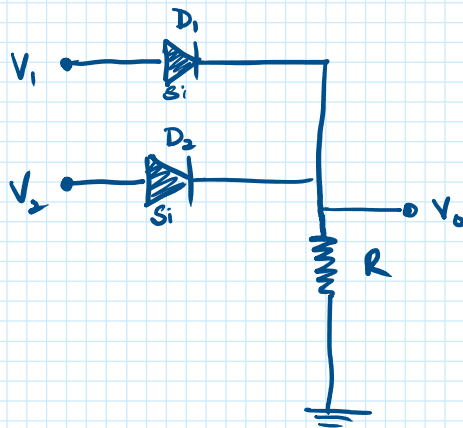


V <sub>1</sub>	V <sub>2</sub>	V <sub>0</sub>
0V [0]	0V [0]	0V [0]
0V [0]	5V [1]	4.3V [1]
5V [1]	0V [0]	4.3V [1]
5V [1]	5V [1]	4.3V [2]

equivalent logic levels

#### • AND GATE

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

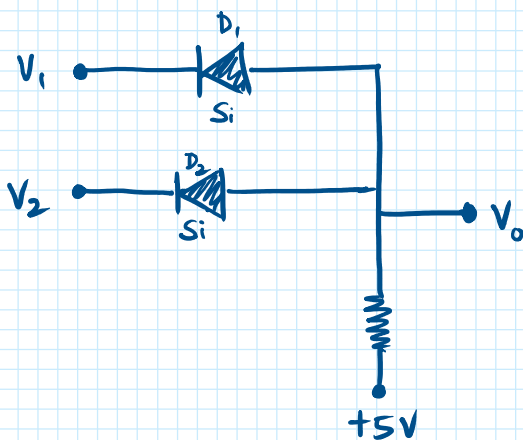

V <sub>1</sub>	V <sub>2</sub>	V <sub>0</sub>
0V [0]	0V [0]	0.7V [0]
0V [0]	5V [1]	0.7V [0]
5V [1]	0V [0]	0.7V [0]
5V [1]	5V [1]	5V [1]

EDA tools :  
to check analysis  
of circuits  
LTspice

### TRANSISTORS

"transfer + resistance"


Transfer of current from a low resistance region to a high resistance region

## Transfer + resistance

Transfer of current from a low resistance region to a high resistance region
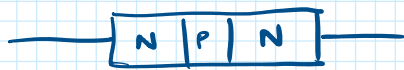
### ① BIPOLAR JUNCTION TRANSISTOR (BJT)







- Three terminal devices
- Constructed by connecting two p-n junctions back to back



- p-type/n-type sandwiched between two of its opposite types
- Bipolar  $\xrightarrow{\text{why}}$  both majority and minority carrier actively participate in its operation
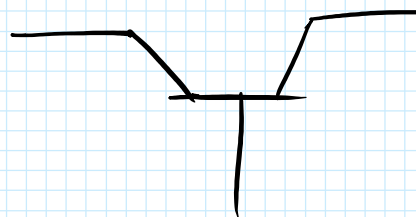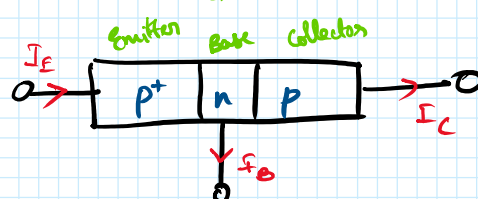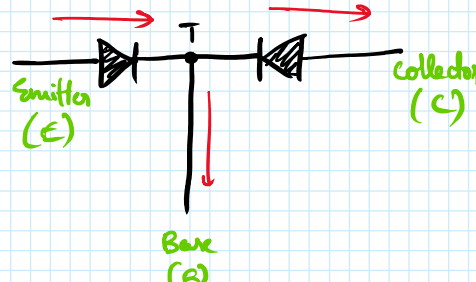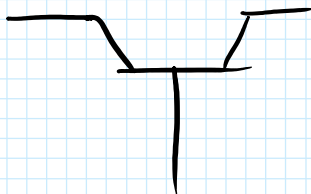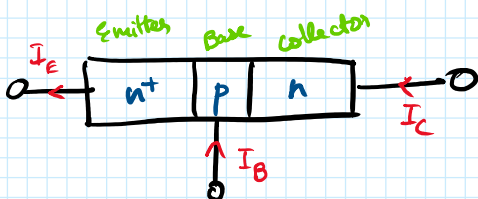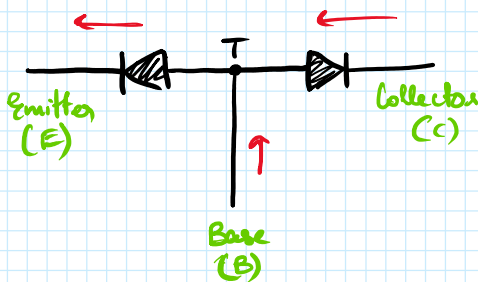
### Terminals

Three terminals: Emitter, base, collector



NOTE

$p^+, n^+ \rightarrow$  more doped

### EMITTER (E)

- supplies charge carriers
- heavily doped
- moderate in size

### BASE (B)

- middle portion; forms two p-n junctions b/w E, C
- lightly doped
- smallest in width

### COLLECTOR (C)

- collects charge carriers
- moderately doped
- widest of all regions; maximum heat dissipated

- moderate 'in size

- lightly doped
- smallest in width
- controls no. of charge carriers emitted

- widest of all regions; maximum heat dissipated here

## TRANSISTOR BIASING

- Transistor has two p-n junctions:
  - ① Emitter - base (EB)
  - ② Collector - base (CB)
- Each of these can be biased independently

Thus we have the following regions of operation:

	EB junction	CB junction	Application
Active region (common)	Forward	Reverse	works as amplifier
Saturation region	Forward	Forward	ON - switch (digital)
Cut-off region	Reverse	Reverse	OFF - switch (digital)
Inverse active region (rare)	Reverse	Forward	Attenuator

## ACTIVE REGION

- Emitter current =  $I_E = I_C + I_B$
- Collector current =  $I_C = I_{C(\text{majority})} + I_{C(\text{minority})}$

## NUMERICALS

① In a common base connection,  $I_E = 1 \text{ mA}$ ,  $I_C = 0.95 \text{ mA}$ .  $I_B = ?$

Soln:  $I_E = I_C + I_B$

$$I_B = I_E - I_C$$

$$= 1 - 0.95$$

$$I_B = \underline{\underline{0.05 \text{ mA}}}$$

Input characteristics

